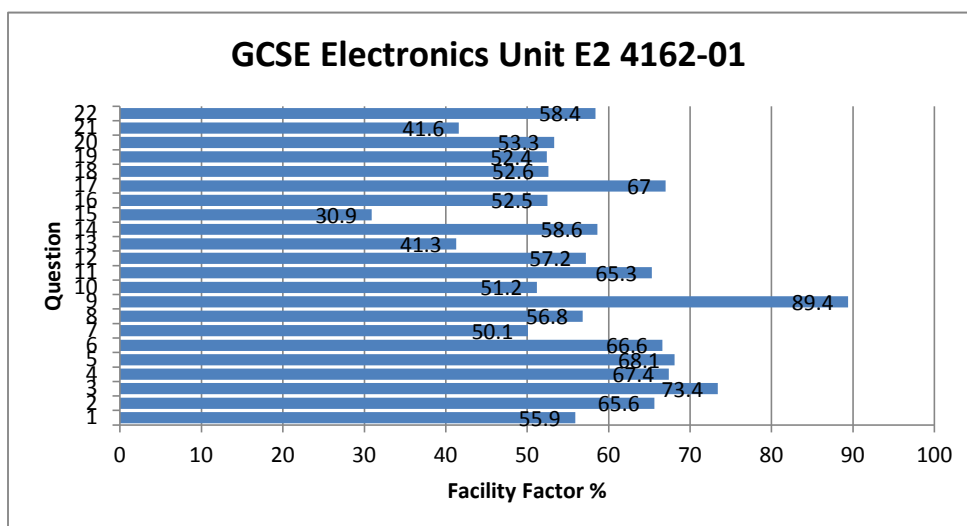


## GCSE Electronics Unit E2 4162-01

All Candidates' performance across questions


Question Title	N	Mean	S D	Max Mark	FF	Attempt %
1	499	0.6	0.5	1	55.9	100
2	499	1.3	0.7	2	65.6	100
3	499	2.2	0.9	3	73.4	100
4	499	2	1.1	3	67.4	100
5	499	0.7	0.5	1	68.1	100
6	499	2	1	3	66.6	100
7	499	0.5	0.5	1	50.1	100
8	499	1.1	0.8	2	56.8	100
9	499	2.7	0.8	3	89.4	100
10	499	1.5	1.2	3	51.2	100
11	499	2	1.2	3	65.3	100
12	499	1.7	0.9	3	57.2	100
13	499	1.7	1.1	4	41.3	100
14	499	2.3	1.5	4	58.6	100
15	499	0.9	1.2	3	30.9	100
16	499	2.1	1.5	4	52.5	100
17	499	1.3	0.8	2	67	100
18	499	1.6	1	3	52.6	100
19	499	1	0.8	2	52.4	100
20	499	1.6	1.3	3	53.3	100
21	499	2.1	1.6	5	41.6	100
22	499	1.2	1	2	58.4	100



10. A rising-edge triggered D-type flip-flop is used for data transfer.

Complete the graphs to show the Q and  $\bar{Q}$  outputs.


[3]

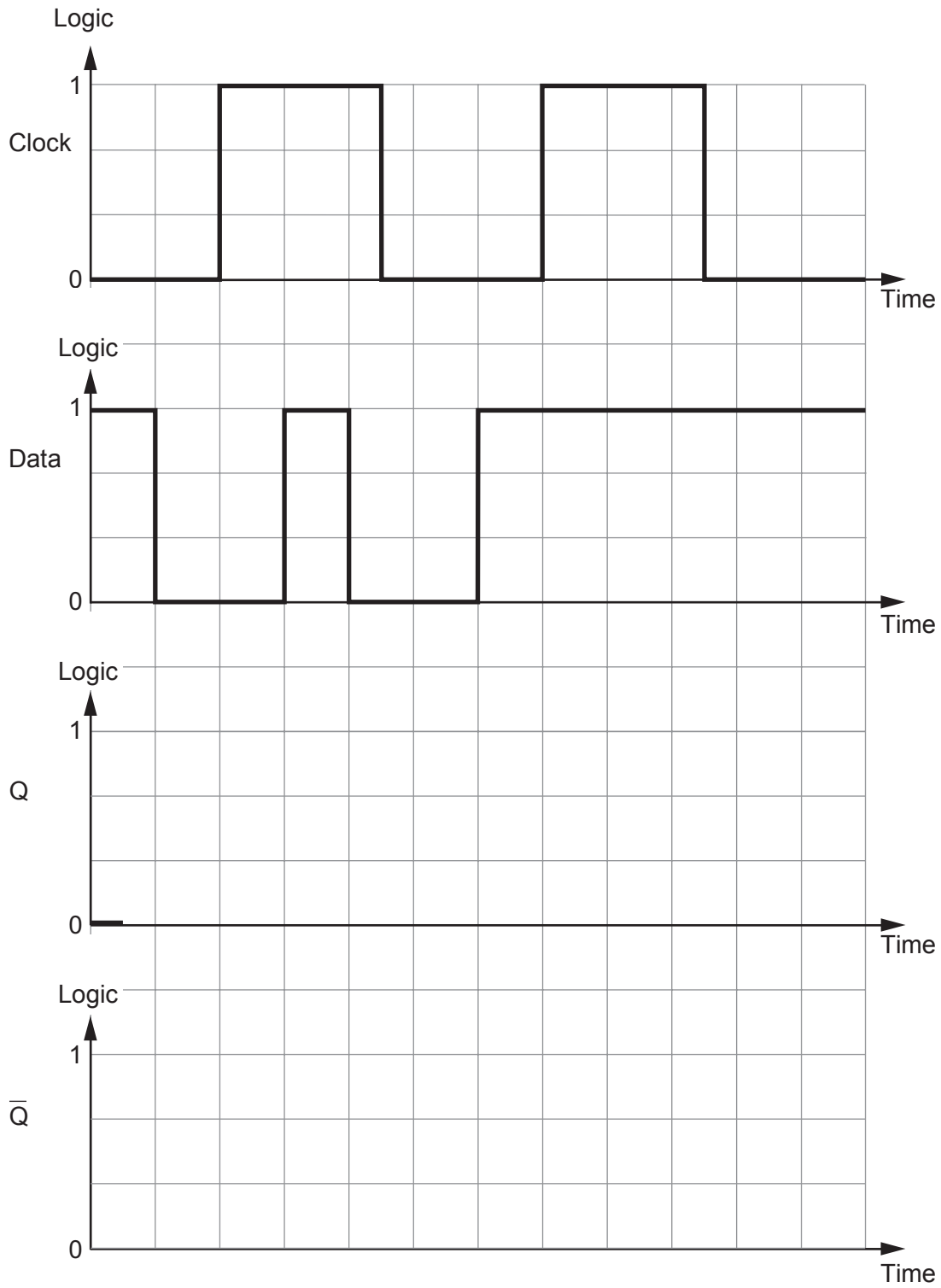

10. A rising-edge triggered D-type flip-flop is used for data transfer.

Complete the graphs to show the Q and  $\bar{Q}$  outputs.

[3]

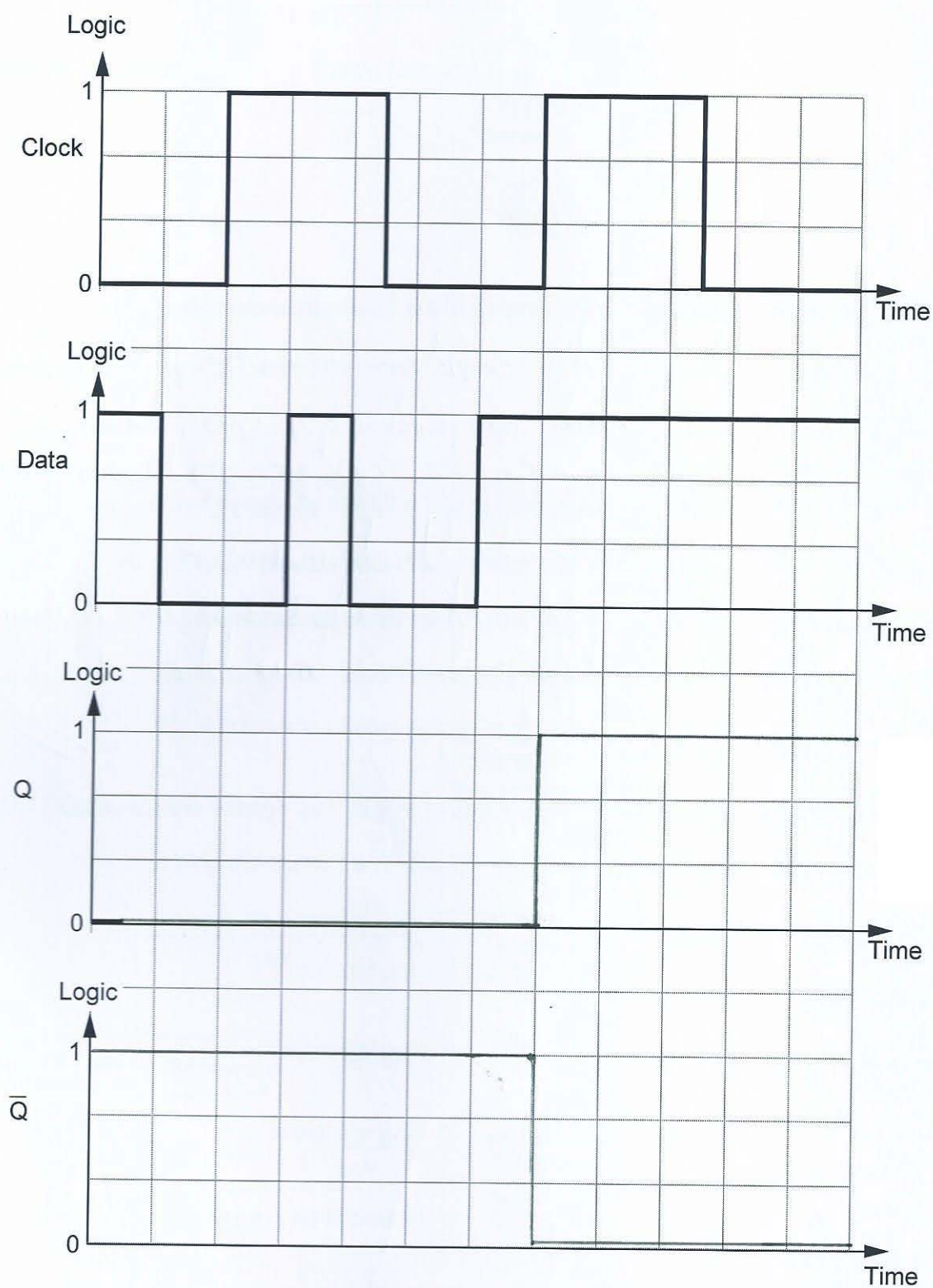


10. A rising-edge triggered D-type flip-flop is used for data transfer.

Complete the graphs to show the Q and  $\bar{Q}$  outputs.

[3]

3

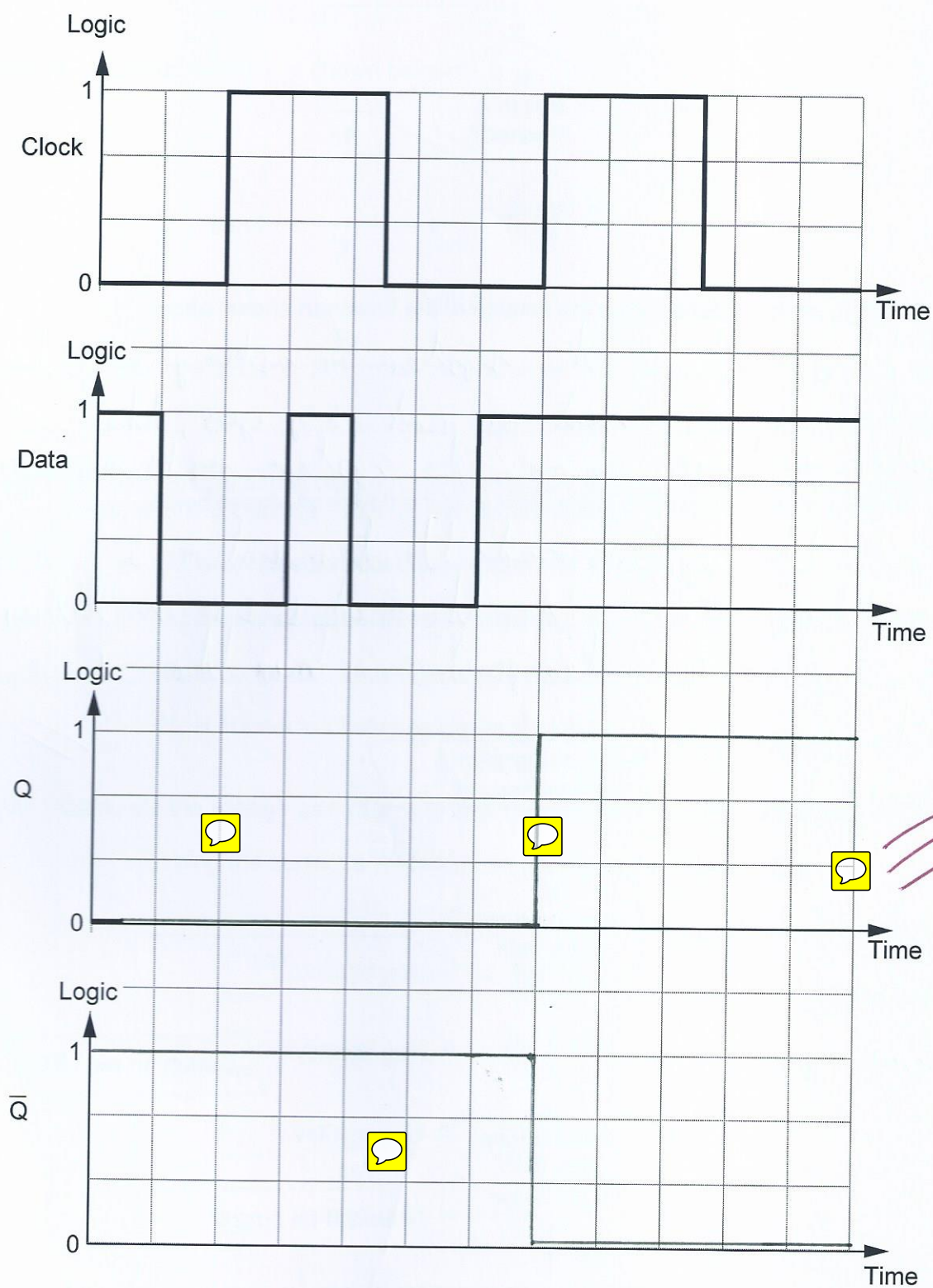
4162  
010011

3

10. A rising-edge triggered D-type flip-flop is used for data transfer.

Complete the graphs to show the Q and  $\bar{Q}$  outputs.

[3]

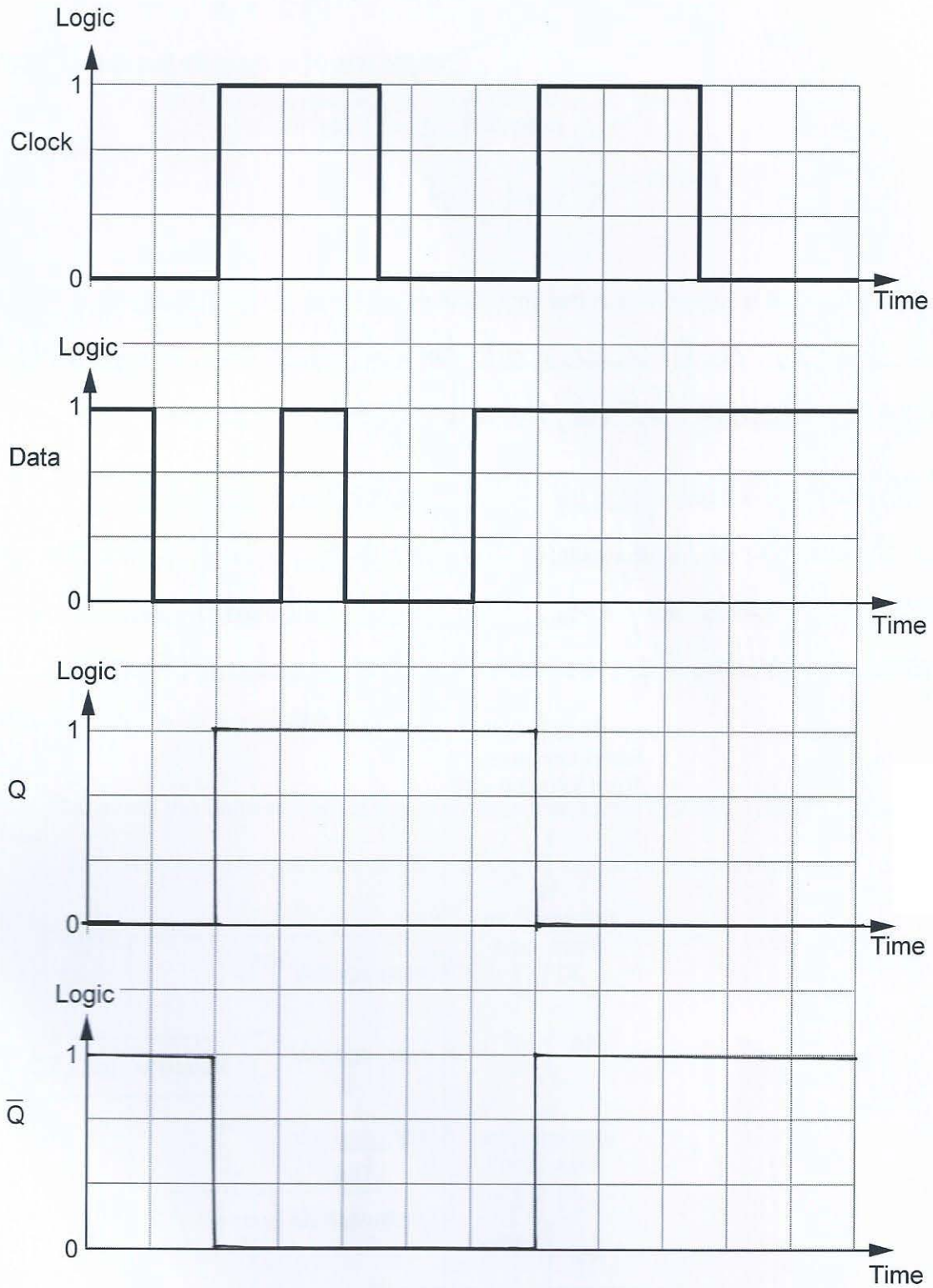




10. A rising-edge triggered D-type flip-flop is used for data transfer.

Complete the graphs to show the Q and  $\bar{Q}$  outputs.


[3]

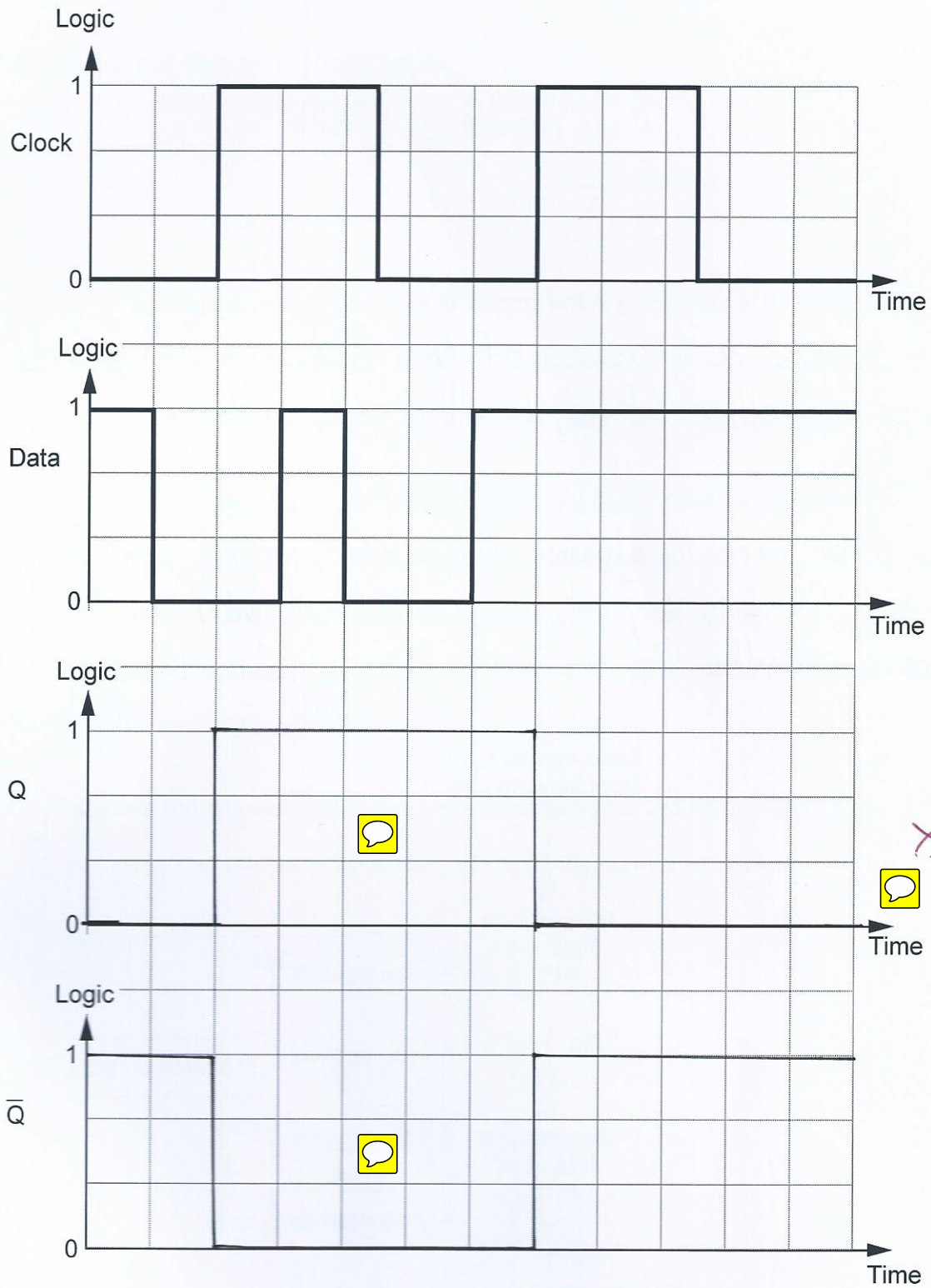

10. A rising-edge triggered D-type flip-flop is used for data transfer.

Complete the graphs to show the Q and  $\bar{Q}$  outputs.


[3]

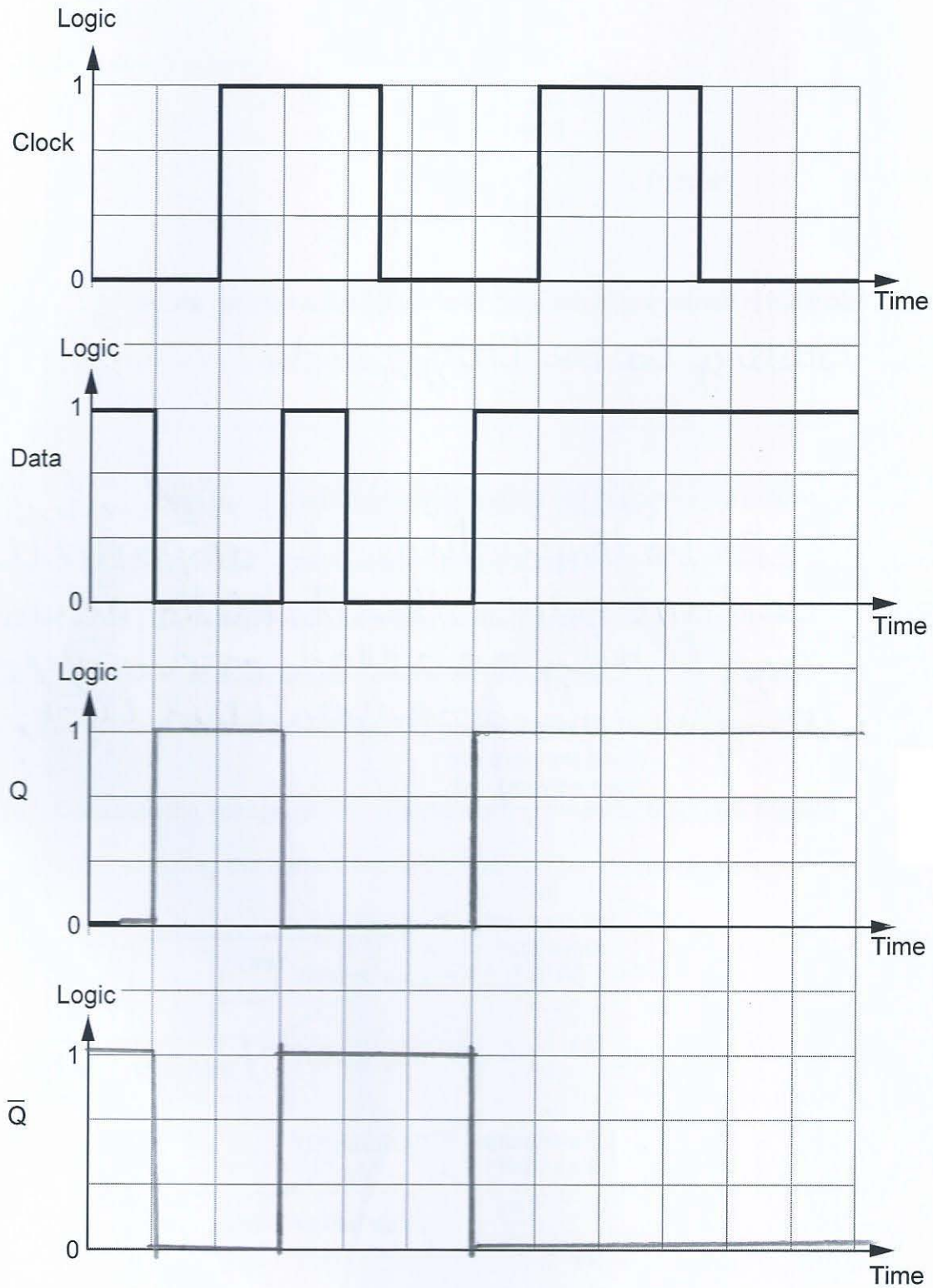

10. A rising-edge triggered D-type flip-flop is used for data transfer.

Complete the graphs to show the Q and  $\bar{Q}$  outputs.

[3]

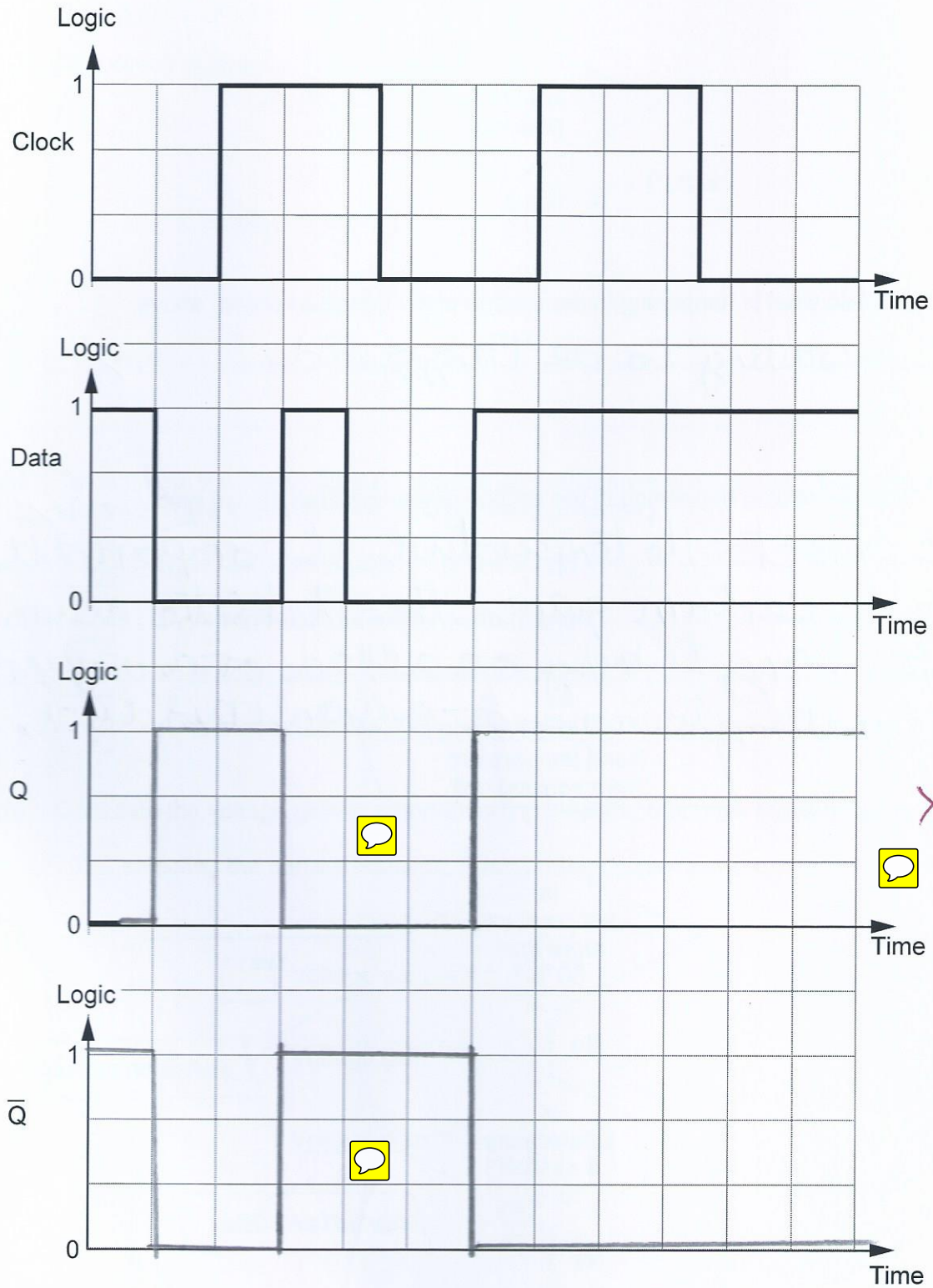

Examiner  
only


4162  
010011



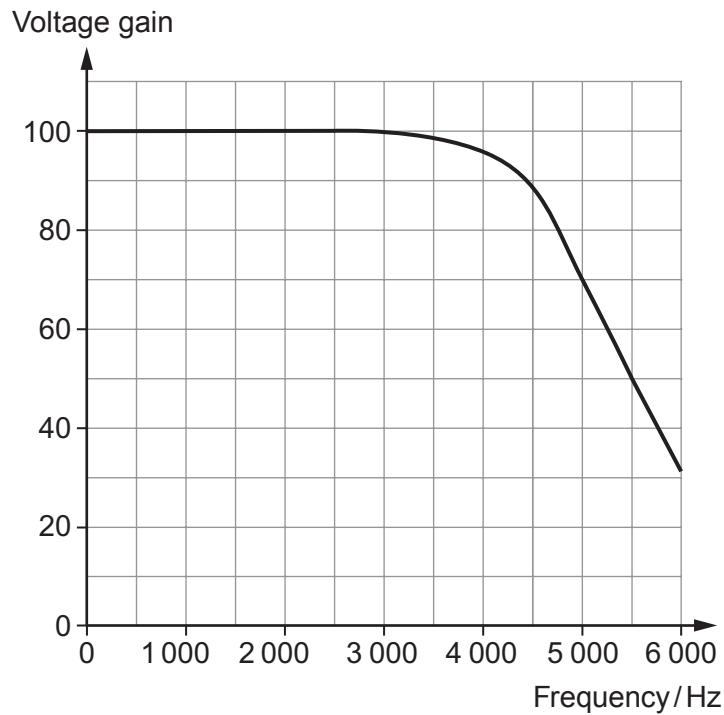18. (a) Which **one** of the following is the best description of the term *bandwidth*?  
(Tick (✓) the correct answer.)

[1]

- ☐ The maximum frequency of the input signal.
- ☐ The input voltage range that can be amplified successfully.
- ☐ The range of frequencies that produces more than a specified voltage gain.
- ☐ The power supply voltage that produces optimum output voltage for a given signal.



- (b) Use the graph to find:

[2]

- (i) the voltage gain at which the bandwidth should be measured;

Voltage gain = .....


- (ii) the bandwidth.

Bandwidth = ..... Hz

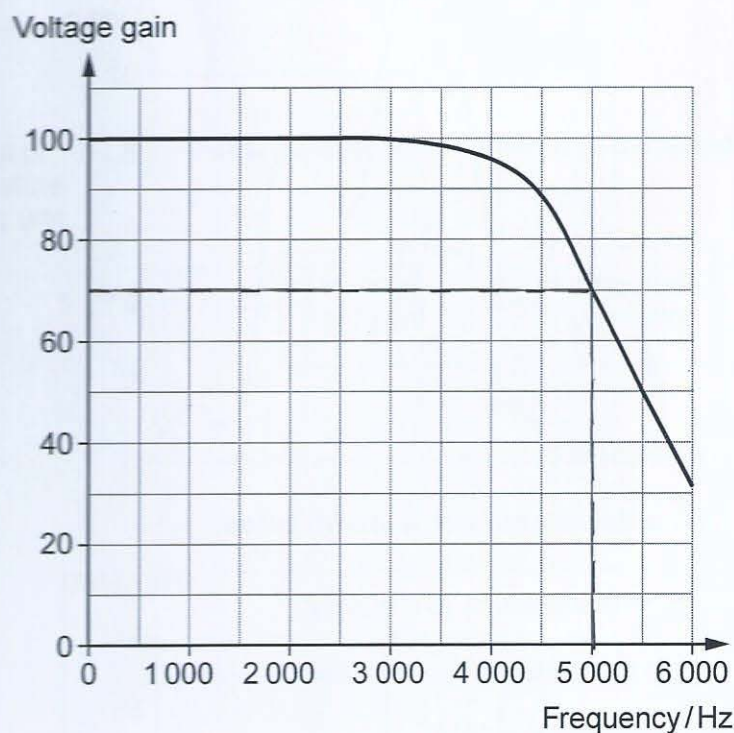18. (a) Which **one** of the following is the best description of the term *bandwidth*?  
(Tick (✓) the correct answer.)

[1]

- ☐ The maximum frequency of the input signal.
- ☐ The input voltage range that can be amplified successfully.
- ☒ The range of frequencies that produces more than a specified voltage gain.
- ☐ The power supply voltage that produces optimum output voltage for a given signal.



- (b) Use the graph to find:

[2]

- (i) the voltage gain at which the bandwidth should be measured;

Voltage gain = 70


- (ii) the bandwidth.

Bandwidth = 5000 Hz

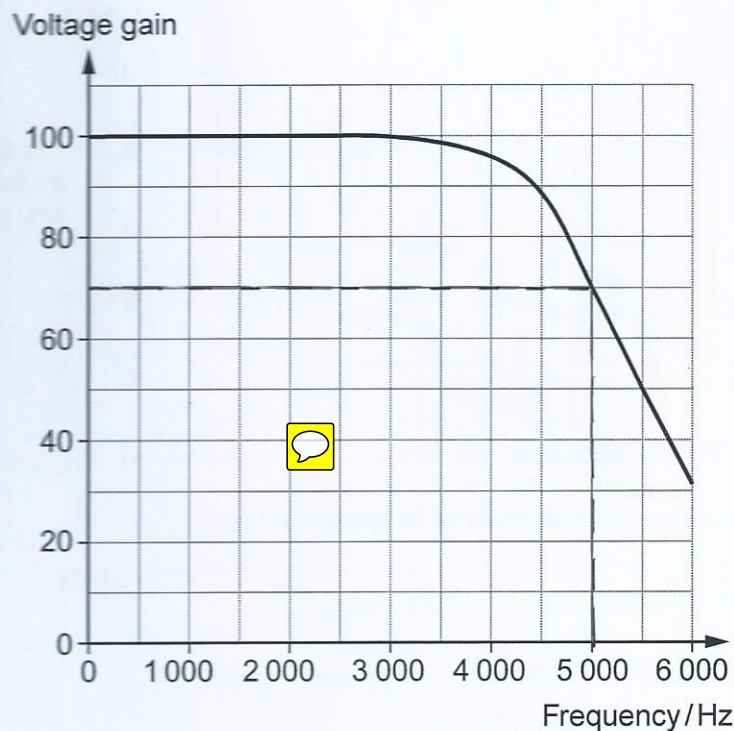18. (a) Which **one** of the following is the best description of the term *bandwidth*?  
(Tick (✓) the correct answer.)

[1]

- ☐ The maximum frequency of the input signal.
- ☐ The input voltage range that can be amplified successfully.
- ☒ The range of frequencies that produces more than a specific voltage gain.
- ☐ The power supply voltage that produces optimum output voltage for a given signal.



- (b) Use the graph to find:

[2]

- (i) the voltage gain at which the bandwidth should be measured;

Voltage gain = 70


- (ii) the bandwidth.

Bandwidth = 5000 Hz

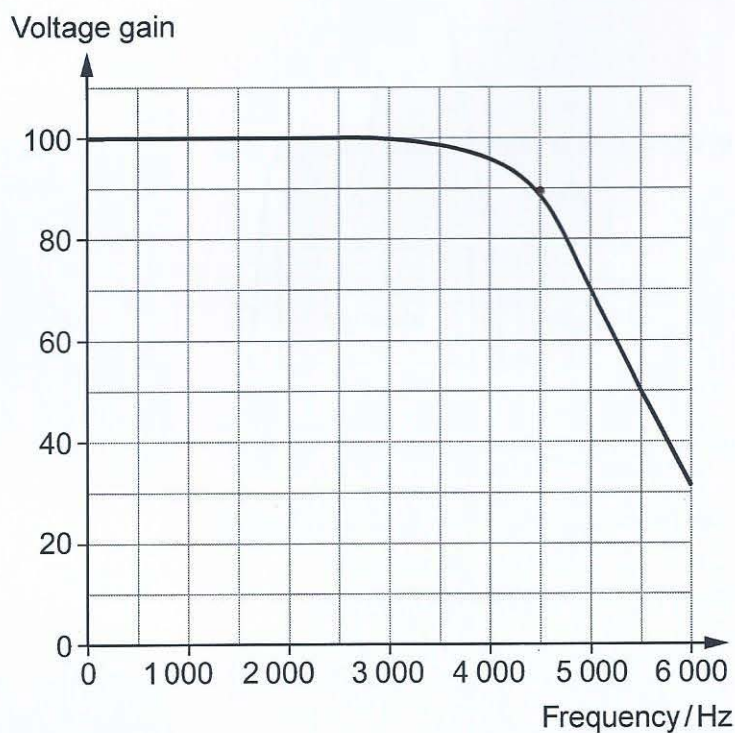18. (a) Which one of the following is the best description of the term *bandwidth*?  
(Tick (✓) the correct answer.)

[1]

- ☐ The maximum frequency of the input signal.
- ☐ The input voltage range that can be amplified successfully.
- ☒ The range of frequencies that produces more than a specified voltage gain.
- ☐ The power supply voltage that produces optimum output voltage for a given signal.



- (b) Use the graph to find:

[2]

- (i) the voltage gain at which the bandwidth should be measured;

Voltage gain =

90

- (ii) the bandwidth.

Bandwidth =

4500


Hz



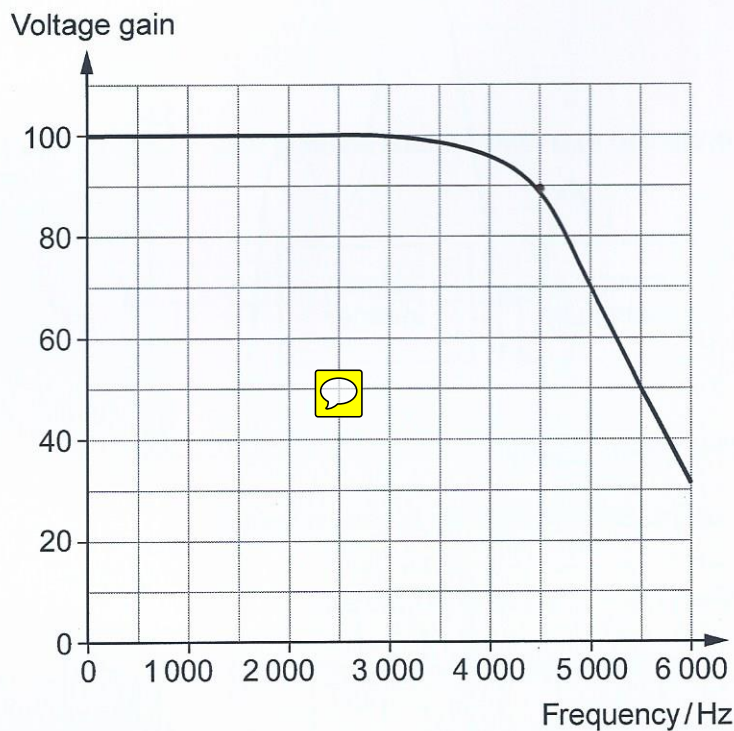18. (a) Which one of the following is the best description of the term *bandwidth*?  
(Tick (✓) the correct answer.)

[1]

- ☐ The maximum frequency of the input signal.
- ☐ The input voltage range that can be amplified successfully.
- ☒ The range of frequencies that produces more than a specified voltage gain.
- ☐ The power supply voltage that produces optimum output voltage for a given signal.



- (b) Use the graph to find:

[2]

- (i) the voltage gain at which the bandwidth should be measured;

Voltage gain =

90

~~30~~

- (ii) the bandwidth.

Bandwidth =



4500


Hz

18. (a) Which **one** of the following is the best description of the term *bandwidth*?  
(Tick (✓) the correct answer.)

[1]

- ☐ The maximum frequency of the input signal.
- ☐ The input voltage range that can be amplified successfully.
- ☒ The range of frequencies that produces more than a specified voltage gain.
- ☐ The power supply voltage that produces optimum output voltage for a given signal.

Voltage gain

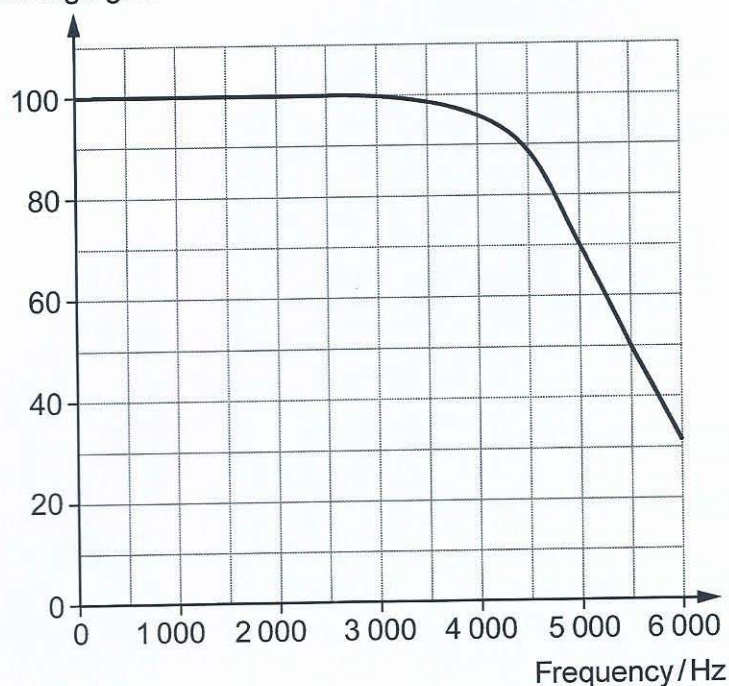

- (b) Use the graph to find:

[2]

- (i) the voltage gain at which the bandwidth should be measured;

$$6000 \div 100.$$

Voltage gain = 60

- (ii) the bandwidth.

$$0.7 \times 100.$$


Bandwidth = 70 Hz

18. (a) Which **one** of the following is the best description of the term *bandwidth*?  
(Tick (✓) the correct answer.)

[1]

- ☐ The maximum frequency of the input signal.
- ☐ The input voltage range that can be amplified successfully.
- ☒ The range of frequencies that produces more than a specified voltage gain.
- ☐ The power supply voltage that produces optimum output voltage for a given signal.

Voltage gain

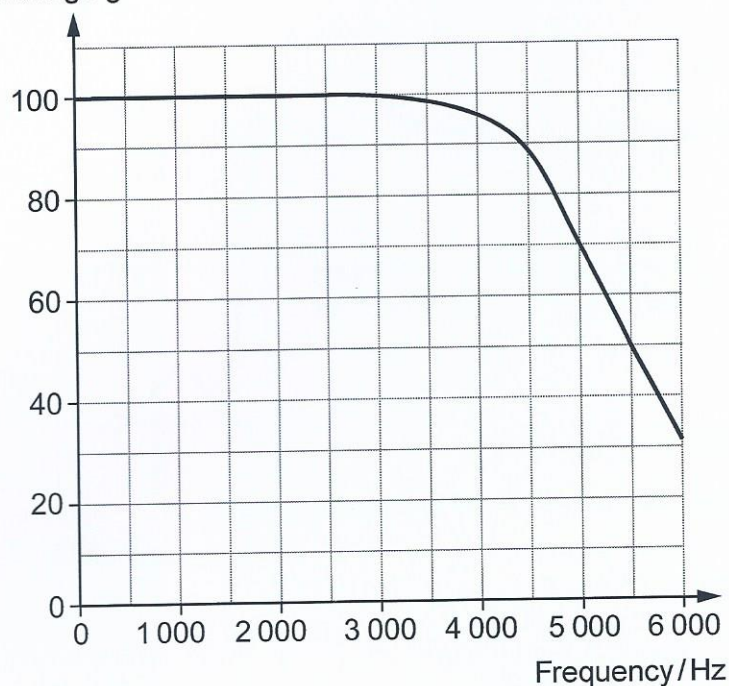

$$\frac{V_{out}}{V_{in}}$$

- (b) Use the graph to find:

[2]

- (i) the voltage gain at which the bandwidth should be measured;

$$6000 \div 100$$



Voltage gain = 60


- (ii) the bandwidth.

$$0.7 \times 100$$



Bandwidth = 70 Hz

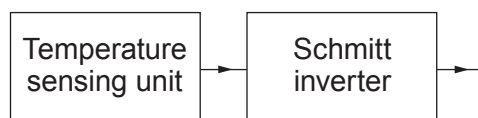20. A Schmitt inverter is connected to a temperature sensing unit.



The circuit runs on a 15V power supply.

Part of the data sheet for the Schmitt inverter is shown below.



When connected to a 15V supply:

- Logic 0 output = 0V;
- Logic 1 output = 15V;
- The output changes from logic 1 to logic 0 when a **rising** input voltage reaches 10 V;
- The output changes from logic 0 to logic 1 when a **falling** input voltage reaches 5V.



The output of the temperature sensing unit is shown in the top graph.

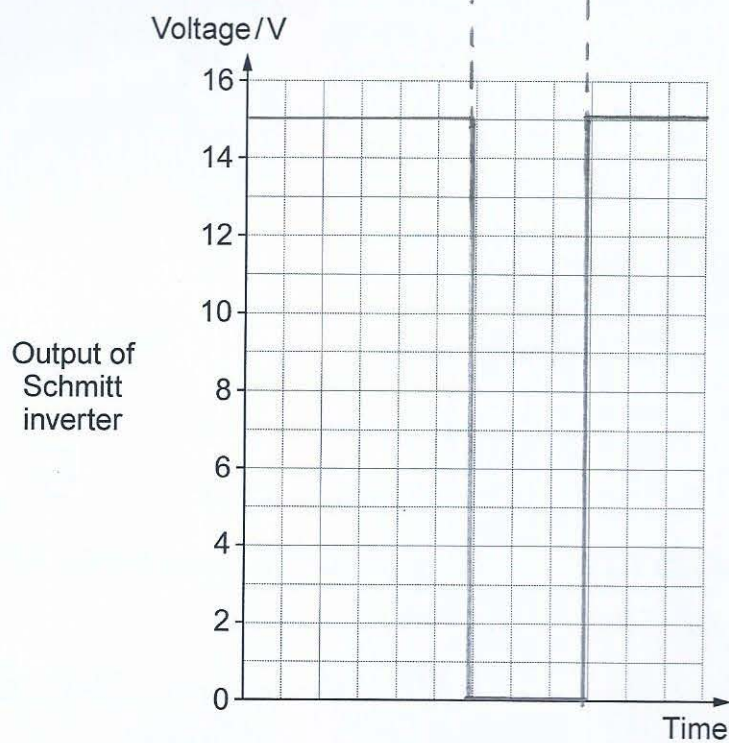
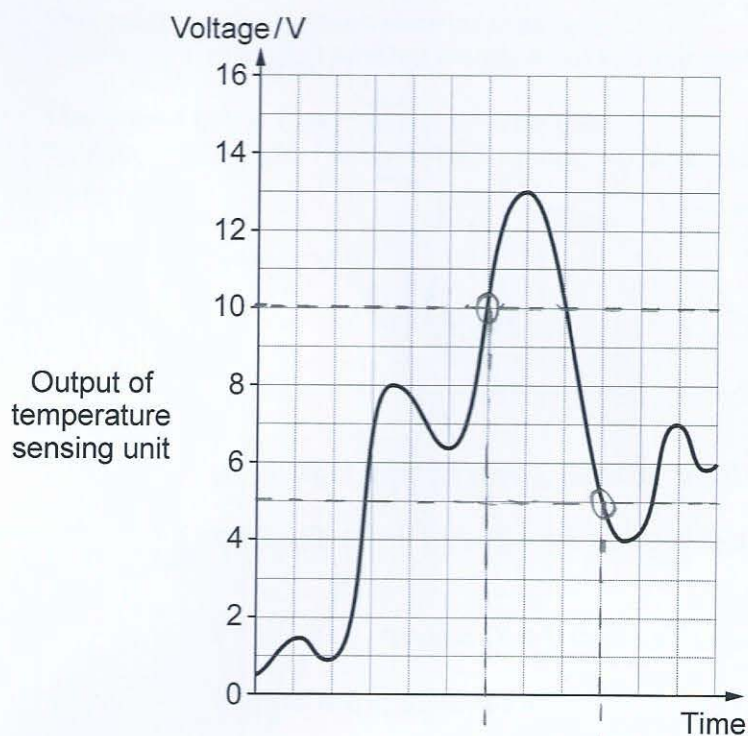
Use the axes provided to draw the corresponding output signal of the Schmitt inverter, when the signal from the temperature sensing unit is applied to its input. [3]



The output of the temperature sensing unit is shown in the top graph.

Use the axes provided to draw the corresponding output signal of the Schmitt inverter, when the signal from the temperature sensing unit is applied to its input.

[3]

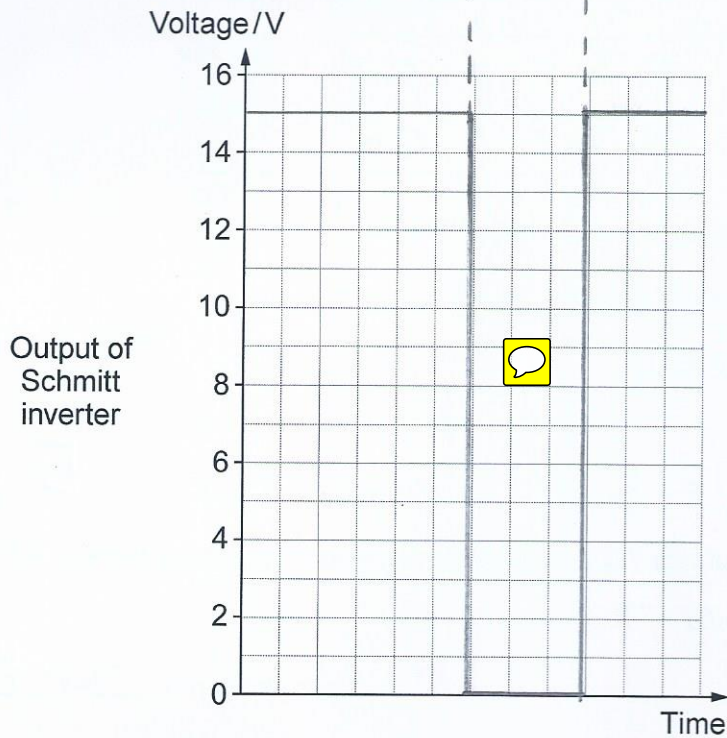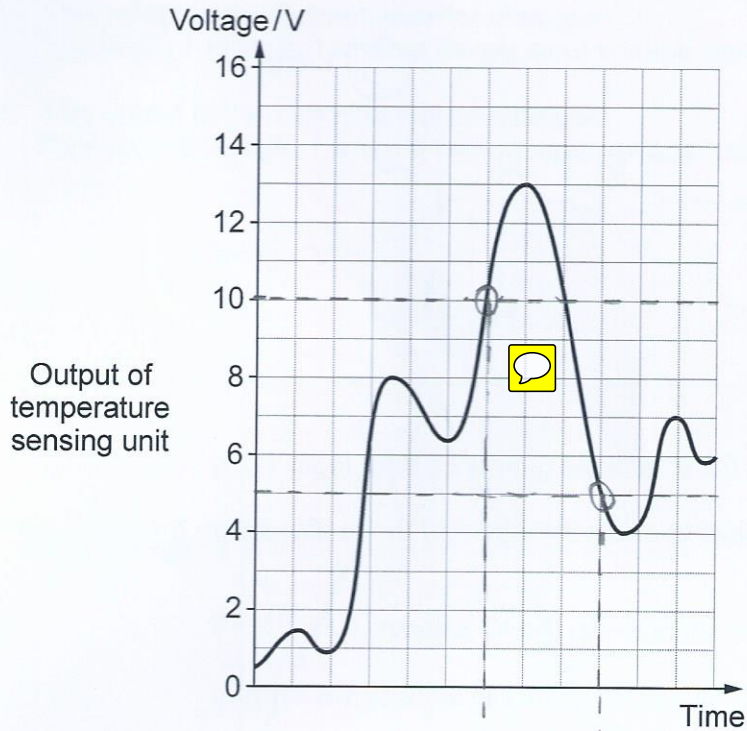



3

4

3

The output of the temperature sensing unit is shown in the top graph.

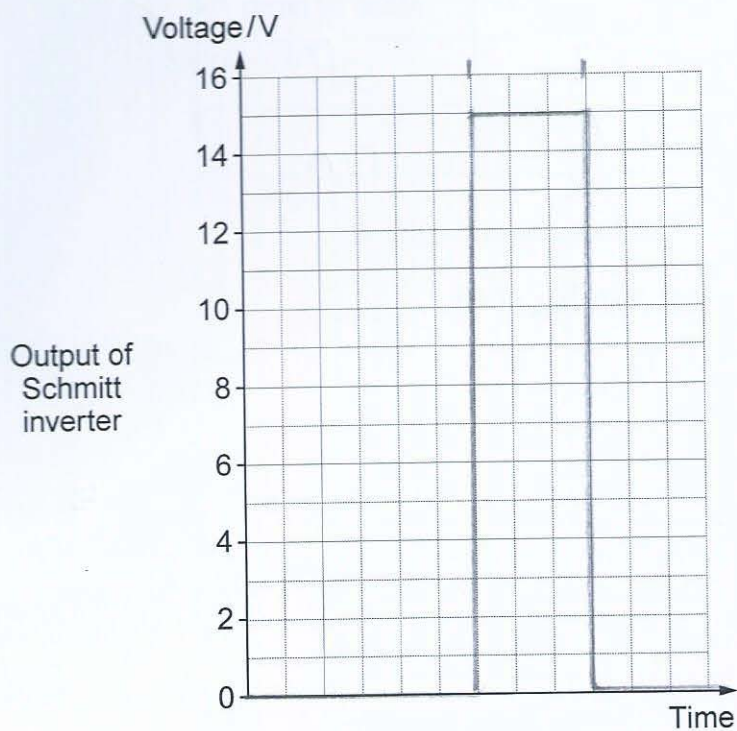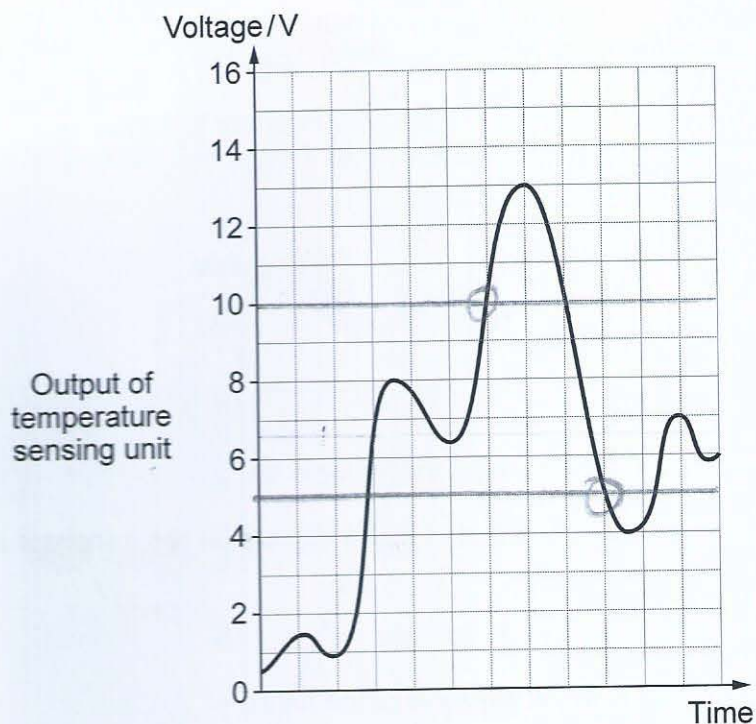Use the axes provided to draw the corresponding output signal of the Schmitt inverter, when the signal from the temperature sensing unit is applied to its input. [3]







The output of the temperature sensing unit is shown in the top graph.

Use the axes provided to draw the corresponding output signal of the Schmitt inverter, when the signal from the temperature sensing unit is applied to its input. [3]

2

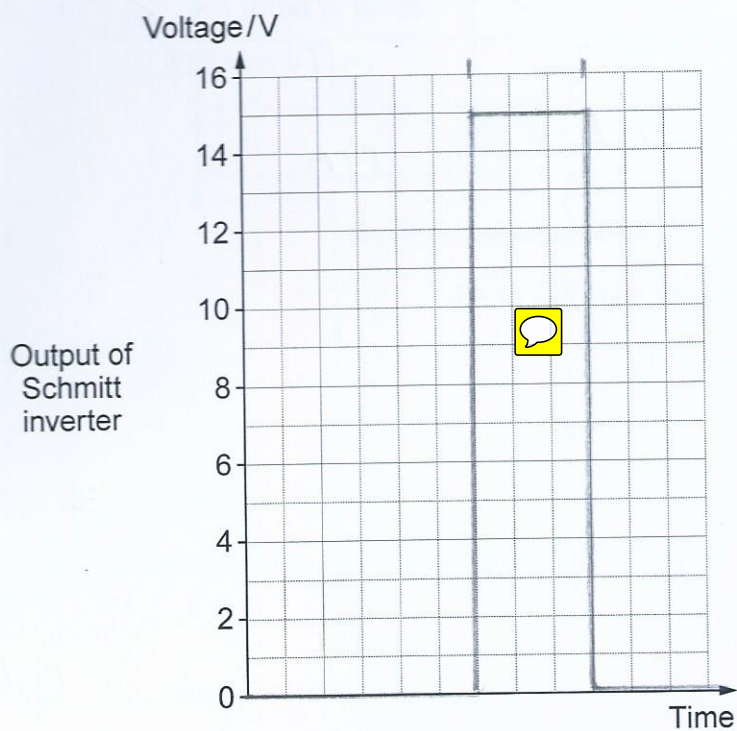
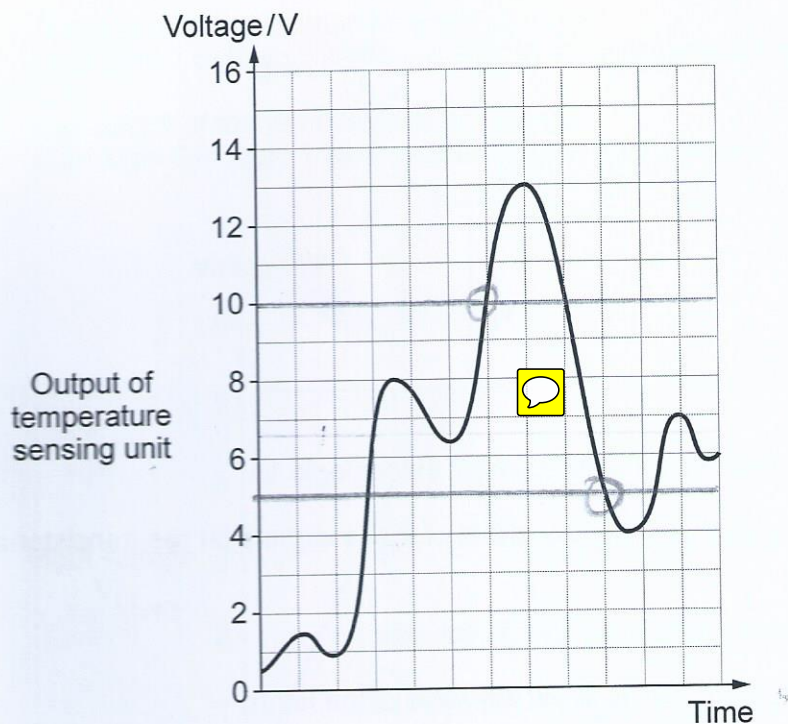


②



The output of the temperature sensing unit is shown in the top graph.

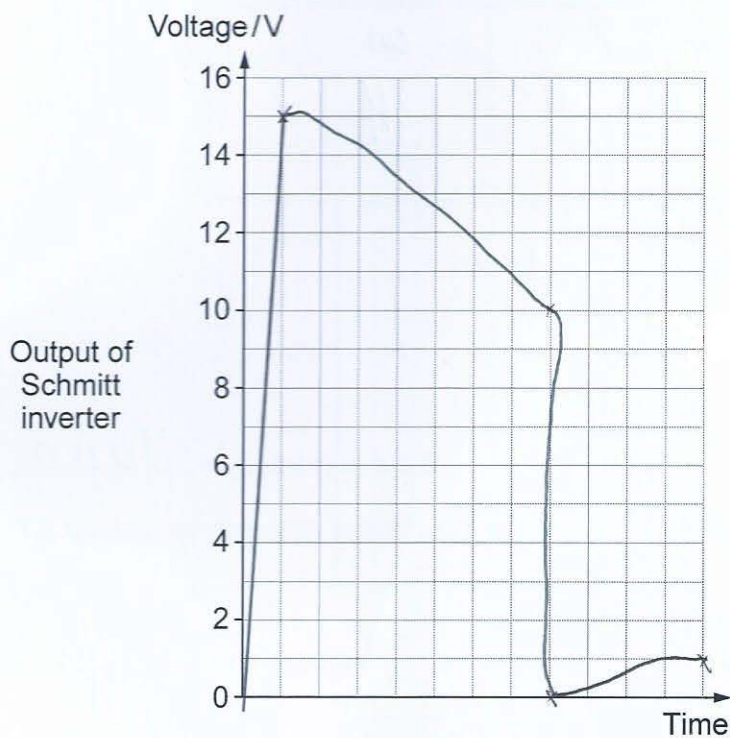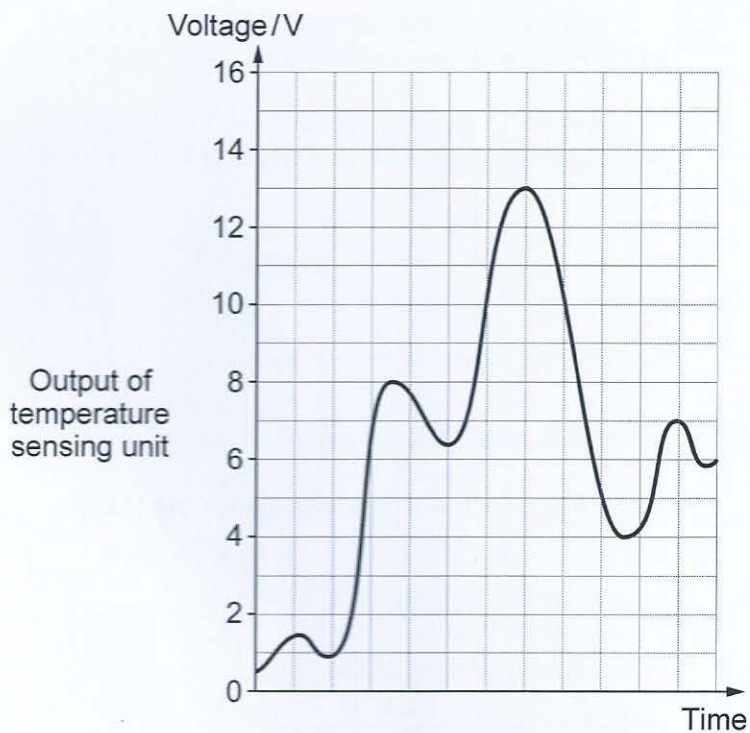Use the axes provided to draw the corresponding output signal of the Schmitt inverter, when the signal from the temperature sensing unit is applied to its input. [3]



The output of the temperature sensing unit is shown in the top graph.

Use the axes provided to draw the corresponding output signal of the Schmitt inverter, when the signal from the temperature sensing unit is applied to its input. [3]

