
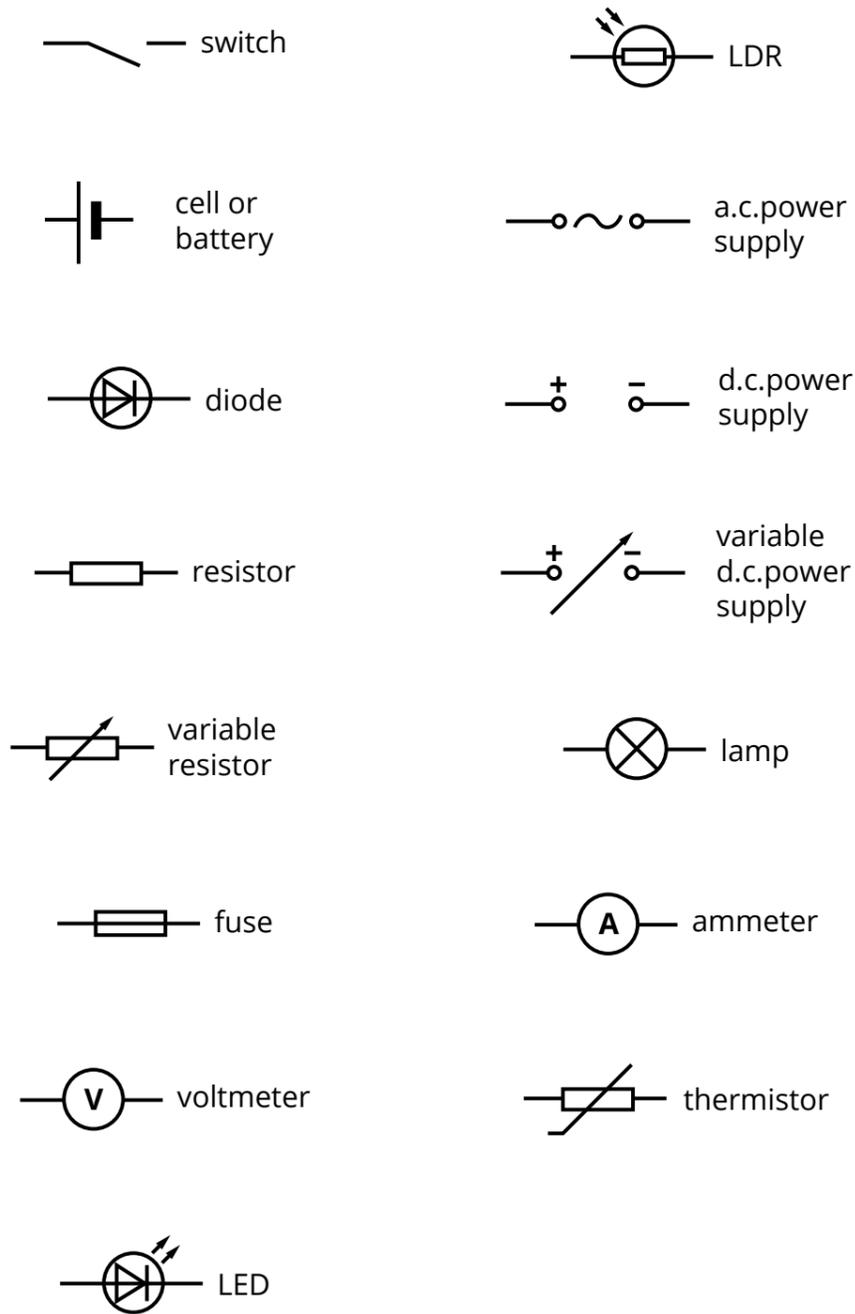


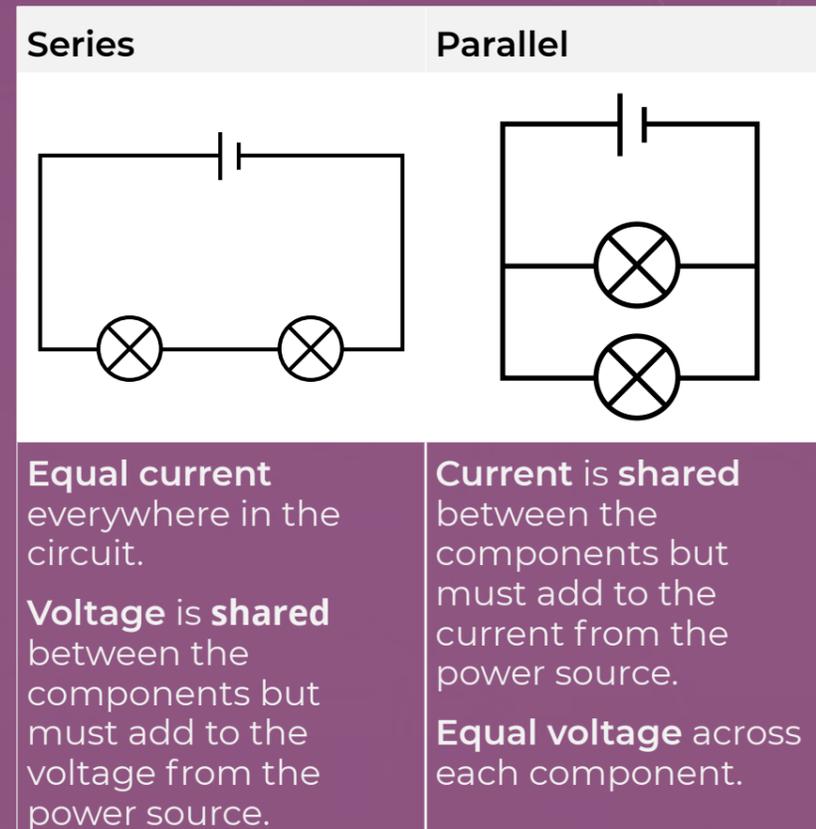The following symbols are used to represent different electrical components:



When you draw a circuit; remember to draw the **correct symbols** in place first then connect using **straight** lines to represent the **wires**.

**Series and parallel circuits**




The **power** of a circuit represents the energy transferred per second. It is measured in Watts where **1W = 1 Joule per second**. These equations can be used to calculate power:

$$\text{Power}(W) = \text{Voltage}(V) \times \text{Current}(A)$$

$$\text{Power}(W) = \text{Current}(A)^2 \times \text{Resistance}(\Omega)$$

$$\text{Energy}(J) = \text{Power}(W) \times \text{Time}(s)$$

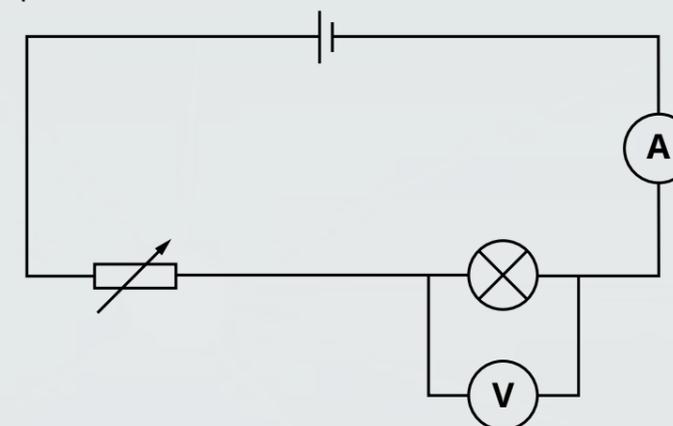This circuit can be used to **investigate how the current changes with voltage** for a bulb. The bulb can be swapped for a resistor or a diode to investigate the relationship with different components.



To get a **series** of values you must record the current and voltage then **adjust the variable resistor** and take the next set of results. You can **repeat** this until you have a complete set.


**Resistors** are used to control or change the current. Fixed resistors are used to lower the current but variable resistors, thermistors and LDRs (light dependent resistors) can change their resistance and change the current.  
**Variable resistors** can be changed by moving a slider or turning a dial, e.g. dimmer switch.  
**Thermistors** change depending on the **temperature**; higher temperature = lower resistance.  
**LDRs** change depending on the **light** on the LDR; brighter light = lower resistance.

**Current** is measured using an **ammeter** which must be connected in **series**.  
**Voltage** is measured using a **voltmeter** which must be connected in **parallel**.

**Resistance** can be calculated using this equation:  

$$\text{Current } (A) = \frac{\text{Voltage } (V)}{\text{Resistance } (\Omega)}$$

Series	Parallel
When you add resistors in series, the resistance increases according to this equation. $R = R_1 + R_2$	When you add resistors in parallel, the resistance of the circuit decreases. $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$

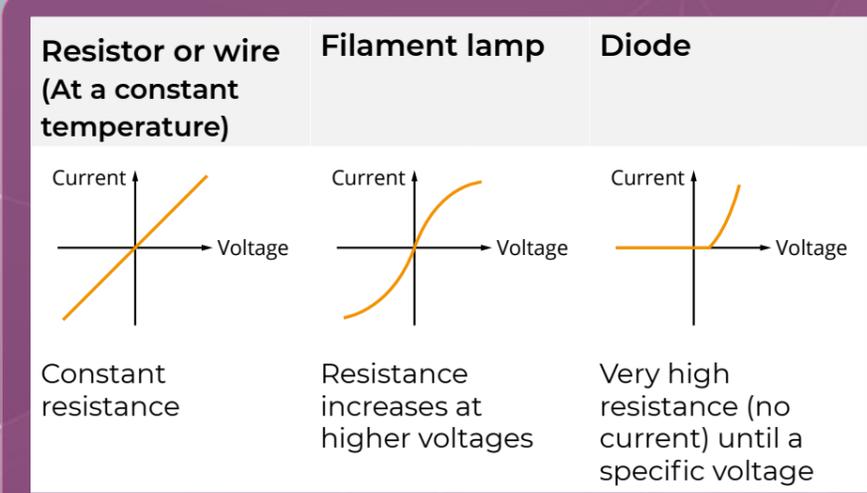

These are the results you would get from each device. You must learn the shape of the curve and be able to describe why it is that shape.